

Your Name	CHEN HE MIN			
Student No.	Z123332			
Circuit	Element in circuit	R or C value		
Sensor circuit	RL for Voltage mode circuit	10 k Ω		
Active Filter	R for determination of cutoff frequency	3.3 k Ω		
	C for determination of cutoff frequency	1 μ F		
	Ra for determination of gain	1 k Ω		
	Rb for determination of gain	7.5 k Ω		
Amplifier	R1 for Amp.	1 k Ω		
	R2 for Amp.	7.5 k Ω		